

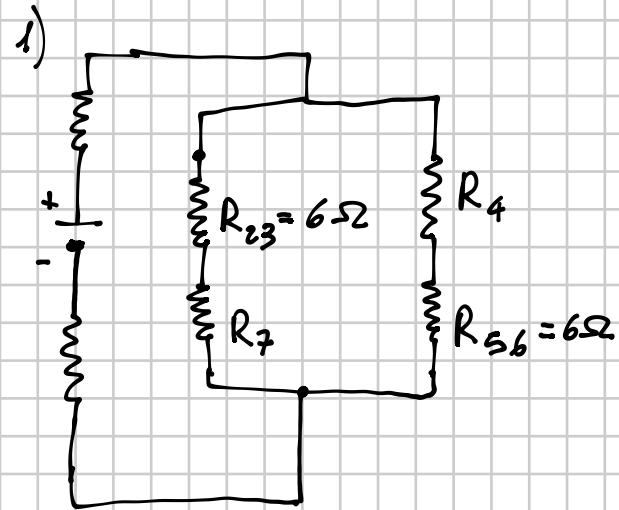


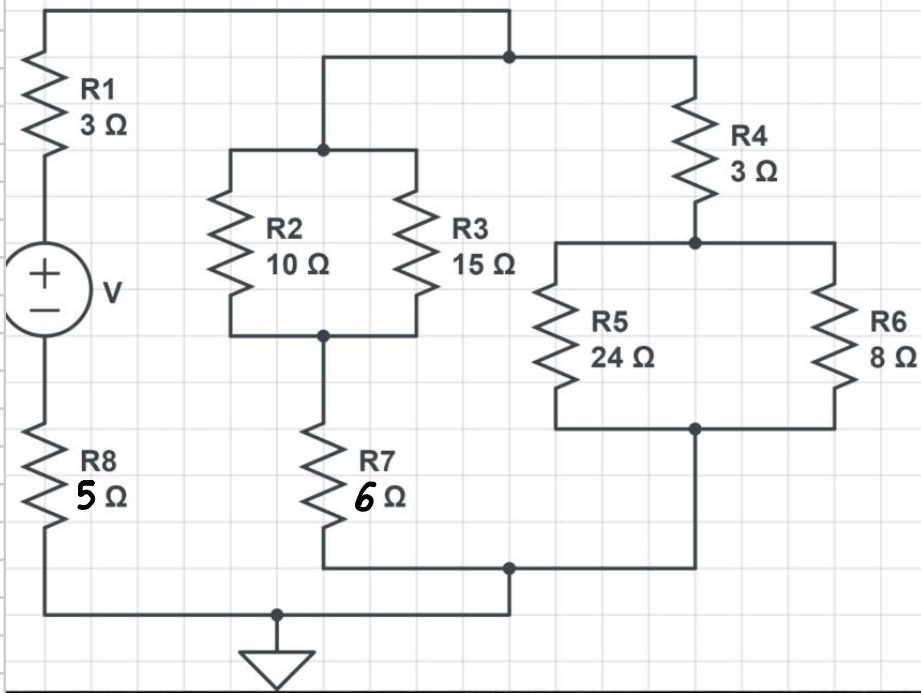CALCOLARE LA RESISTENZA EQUIVALENTE DEL CIRCUITO



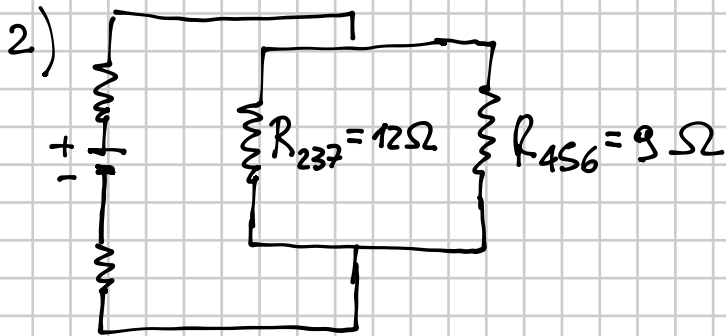
$$R_{23} = \frac{10 \cdot 15}{10 + 15} \Omega = \frac{150}{25} \Omega = 6 \Omega$$



$$R_{56} = \frac{24 \cdot 8}{24 + 8} \Omega = \frac{6 \cdot 24 \cdot 8}{32 \cdot 4} = 6 \Omega$$

$$R_{237} = 6 \Omega + 6 \Omega = 12 \Omega$$
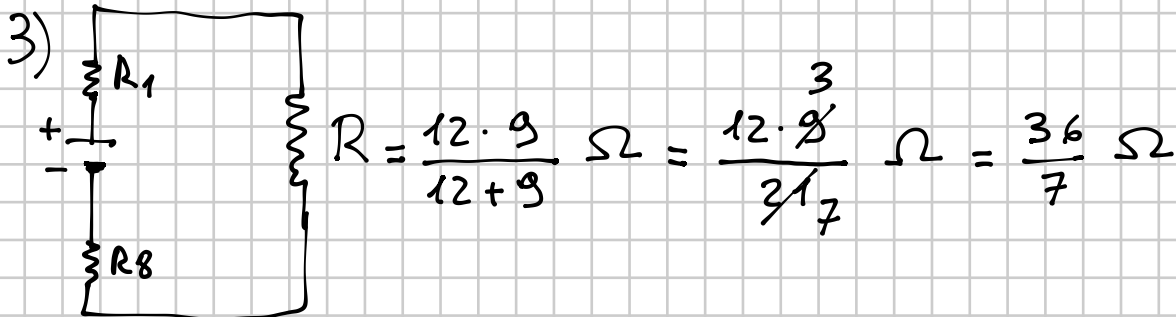
$$R_{456} = 6 \Omega + 3 \Omega = 9 \Omega$$




$$R = \frac{12 \cdot 9}{12 + 9} \Omega = \frac{12 \cdot 9}{21} \Omega = \frac{36}{7} \Omega$$

$$R_{eq} = R_1 + R + R_8 = 3 \Omega + \frac{36}{7} \Omega + 5 \Omega =$$

$$= 8 \Omega + \frac{35}{7} \Omega + \frac{1}{7} \Omega = 13 \Omega + \frac{1}{7} \Omega =$$

$$= 13,142... \Omega \approx 13 \Omega$$

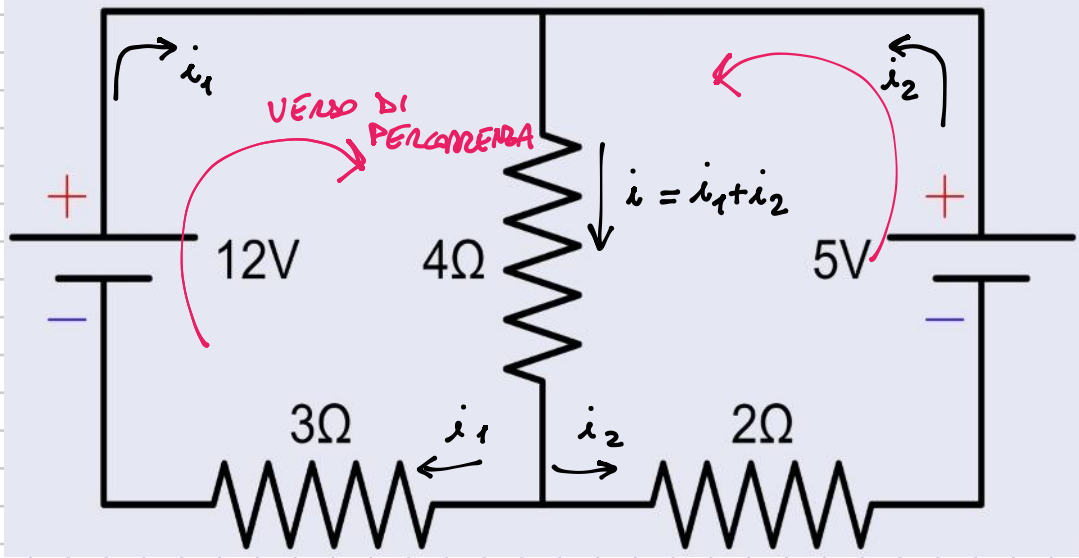

CALCOLARE LE
CORRENTI i, i_1, i_2

$$\begin{cases} i = i_1 + i_2 \\ 12V - (4\Omega)i - (3\Omega)i_1 = 0 \\ 5V - (4\Omega)i - (2\Omega)i_2 = 0 \end{cases}$$

$$\begin{cases} i = i_1 + i_2 \\ 12 - 4i - 3i_1 = 0 \\ 5 - 4i - 2i_2 = 0 \end{cases} \quad \begin{cases} i = i_1 + i_2 \\ 12 - 4(i_1 + i_2) - 3i_1 = 0 \\ 5 - 4(i_1 + i_2) - 2i_2 = 0 \end{cases} \quad \begin{cases} // \\ 12 - 4i_1 - 4i_2 - 3i_1 = 0 \\ 5 - 4i_1 - 4i_2 - 2i_2 = 0 \end{cases}$$

$$\begin{cases} // \\ -7i_1 - 4i_2 = -12 \\ -4i_1 - 6i_2 = -5 \end{cases} \quad \begin{cases} // \\ 7i_1 + 4i_2 = 12 \\ 4i_1 + 6i_2 = 5 \end{cases} \quad \begin{cases} // \\ i_2 = \frac{12 - 7i_1}{4} \\ 4i_1 + \frac{3}{4} \cdot \frac{12 - 7i_1}{1} = 5 \end{cases}$$

$$\Downarrow \\ 8i_1 + 36 - 21i_1 = 10$$

$$\begin{cases} i = i_1 + i_2 = 1,5 A \\ i_1 = 2 A \\ i_2 = \frac{12 - 14}{4} = -0,5 A \end{cases} \quad \begin{cases} -13i_1 = -26 \\ i_1 = 2 A \end{cases}$$

← siccome i_2 è negativo, significa che il verso di i_2 è opposto a quello ipotizzato all'inizio